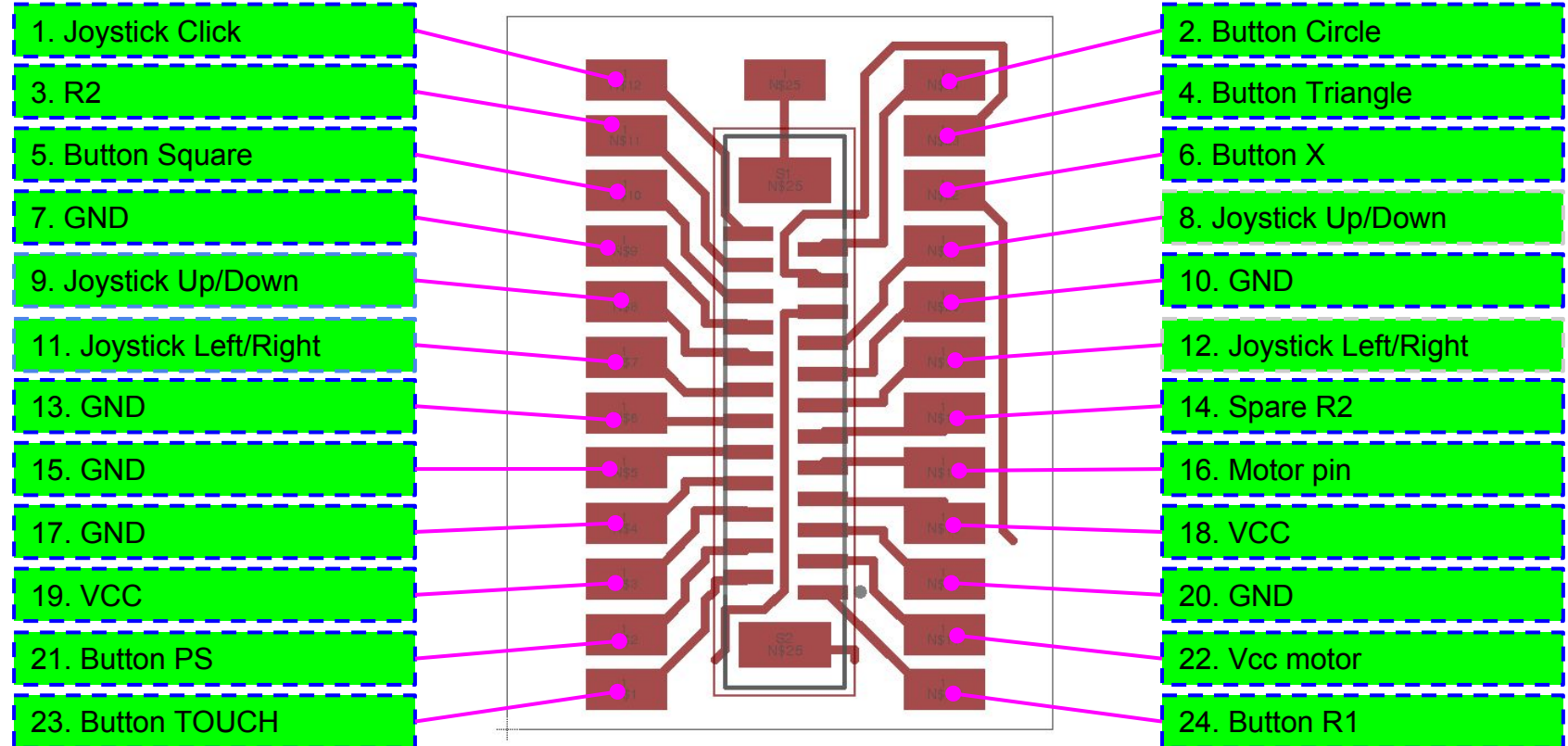



Playstation Aim Controller

Reverse engineering


Main board to PCB




PCB to Trigger Controller (Back)

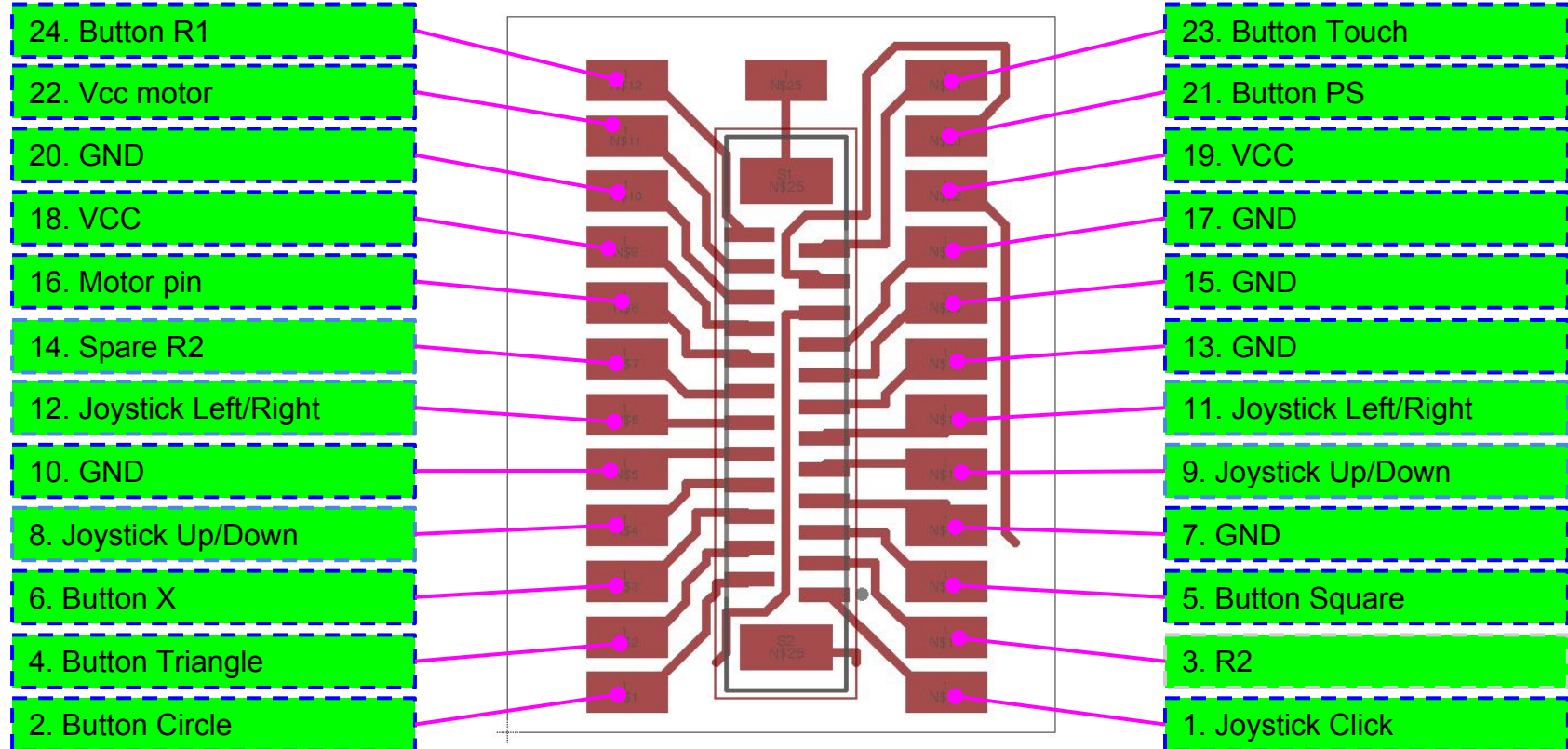



PCB to Front Controller

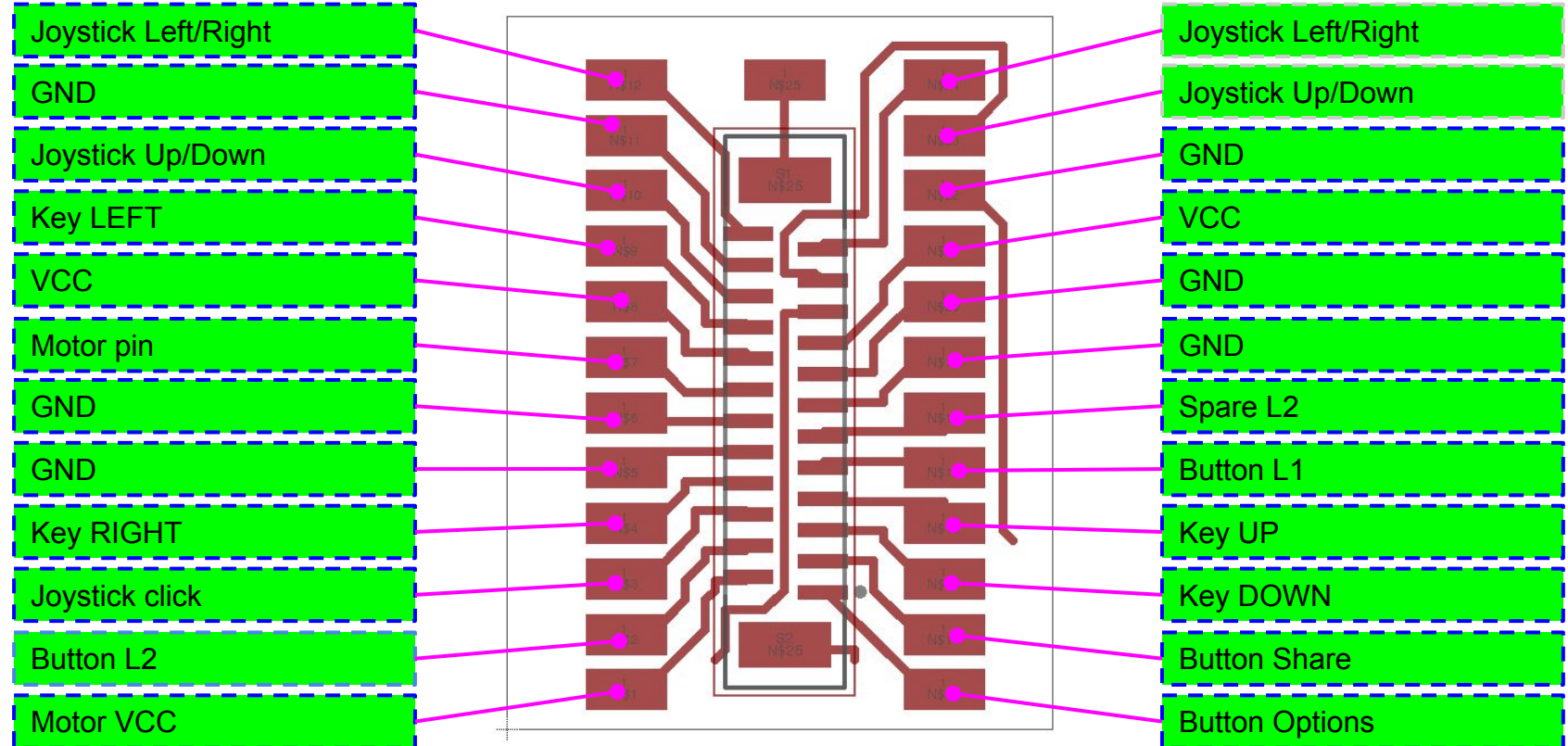

Main board to PCB

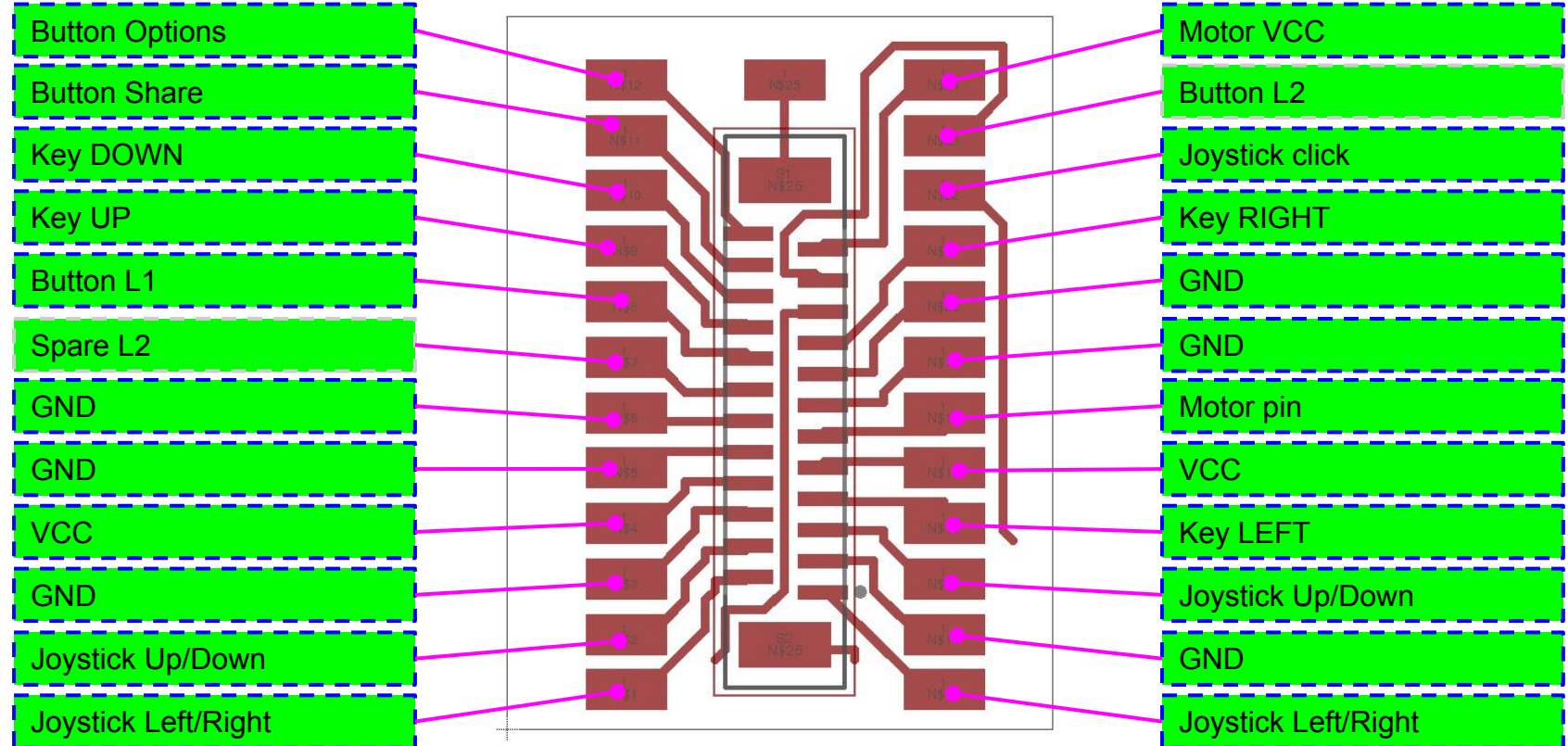

Teensy 3.6 pin outs

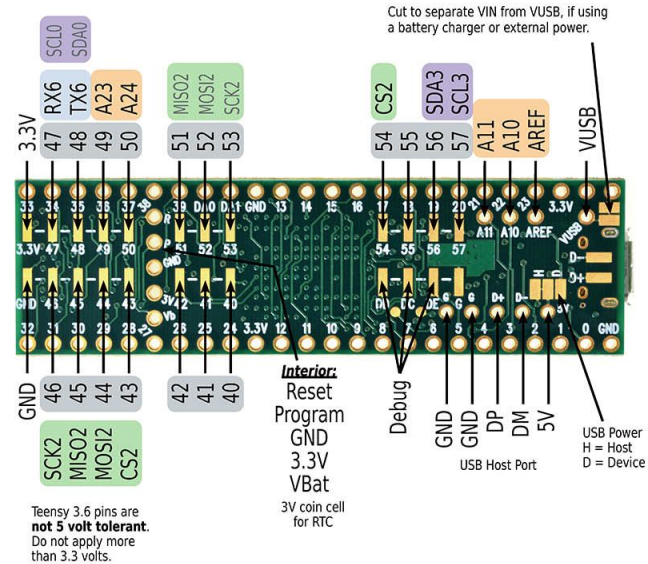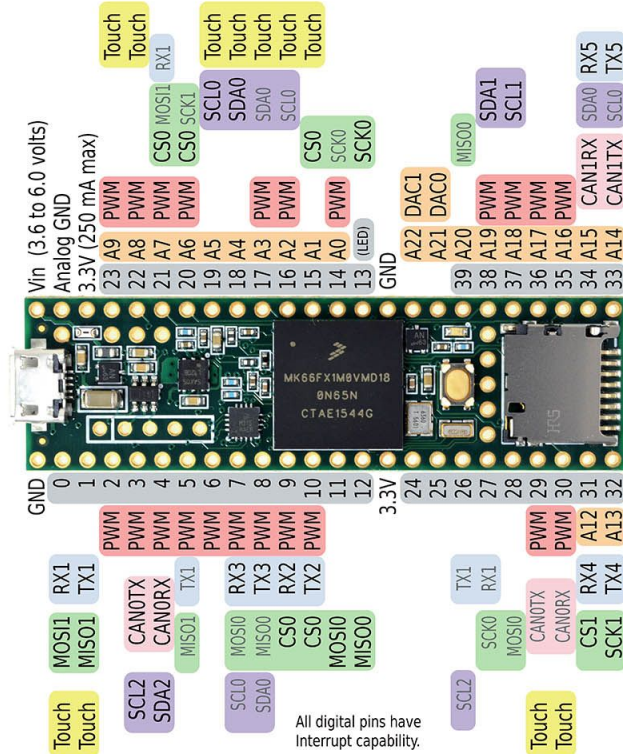

Share | Direct

Left/Right | In: 20 Out:
MCP 38

Up/Down | In: 21 Out: MCP
38

Left | In: 3 Out: 4


Down | In: 5 Out: 6

Options | Direct

Click | In: 42 Out: 43

Up | In: 9 Out: 10

Right | In: 7 Out: 8

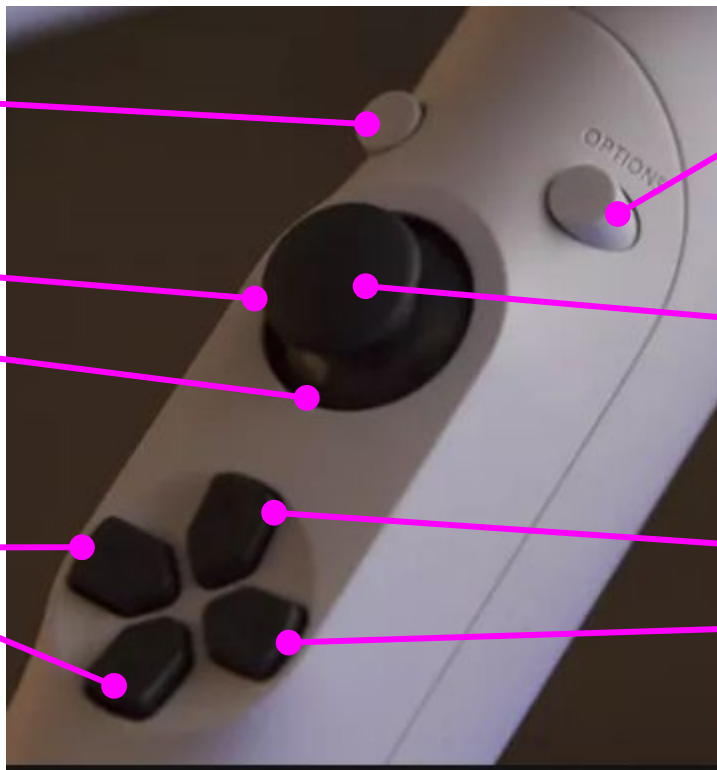

L1 | In: 40 Out: 41



L2 | In: 39 Out: MCP 36

PS | Direct

Triangle | In: 30 Out: 31

Left/Right | In: 23 Out: MCP
37

Up/Down | In: 22 Out: MCP
37

Square | In: 26 Out: 27



Touch | In: 44 Out: 45

Click | In: 32 Out: 33

Circle | In: 28 Out: 29


X | In: 24 Out: 25

R1 | In: 34 Out: 35




R2 | In 14 Out: MCP 36

Digital potentiometer for R2 and L2

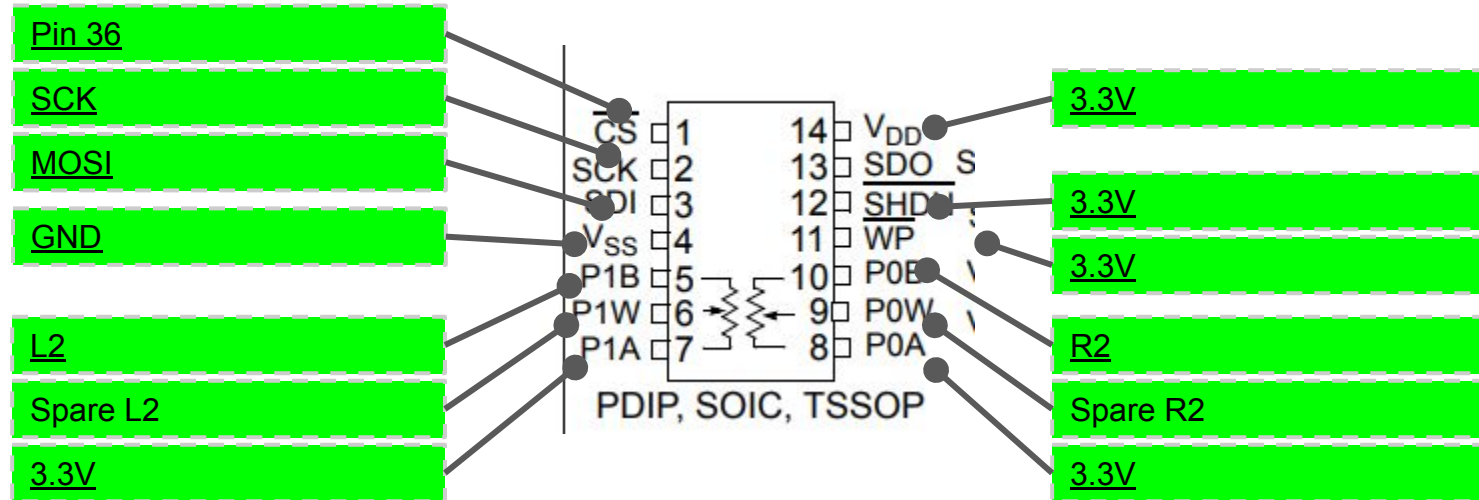

Digital potentiometer for Back Joystick

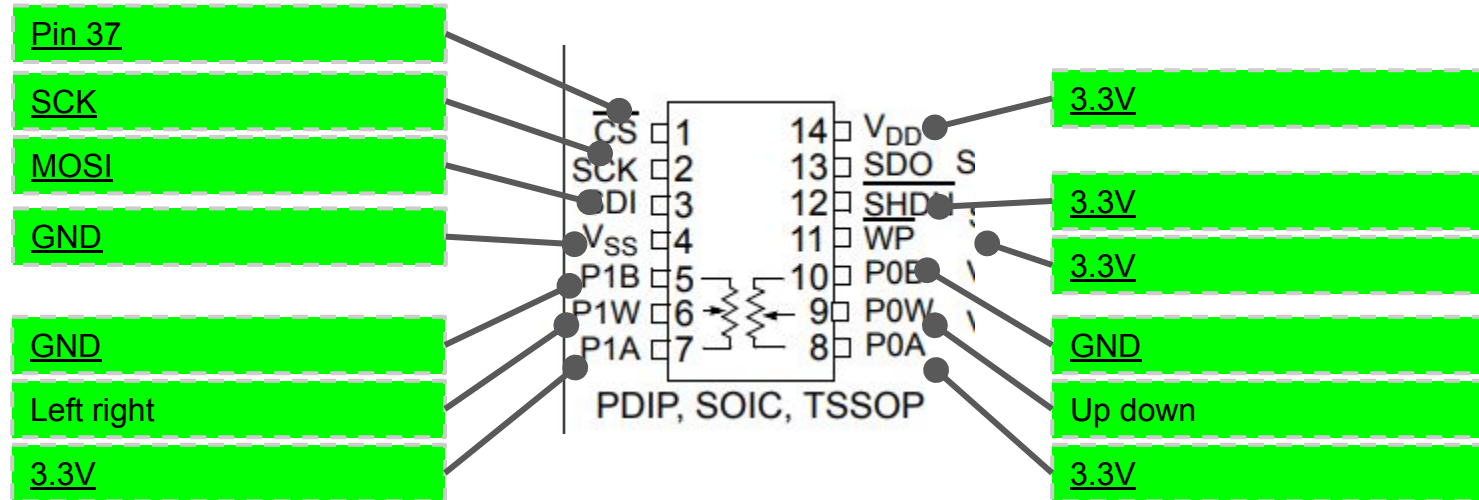

Digital potentiometer for Front Joystick

